

EVENING
08 MAR 2021

[Total no. of Questions:09]
Uni. Roll No.

[Total No. of Pages:02]

B.Tech (Batch 2018 onwards)
Sem.-3rd
ELECTRICAL CIRCUIT ANALYSIS
SUBJECT CODE: PCEE-101
PAPER ID:- 16064

Time: 03 Hours

Maximum Marks:60

Instructions to Candidates


- 1) Parts A and B are Compulsory
- 2) Part C has Two Questions Q8 and Q9. Both are compulsory, but with internal choice.
- 3) Any missing data may be assumed appropriately

Part-A

[Marks:02 each]

Q1.

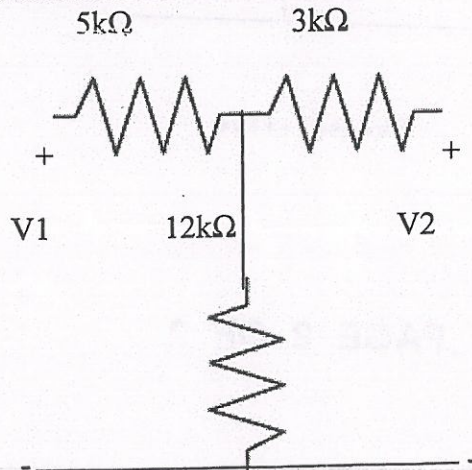
- a) What is duality?
- b) Define transient state response.
- c) Define admittance.
- d) Define convolution integral.
- e) Obtain Laplace transform of $f(t) = 1 - e^{-at}$, a being a constant.
- f) Find Z parameters for network shown:



Part-B

[Marks:04 each]

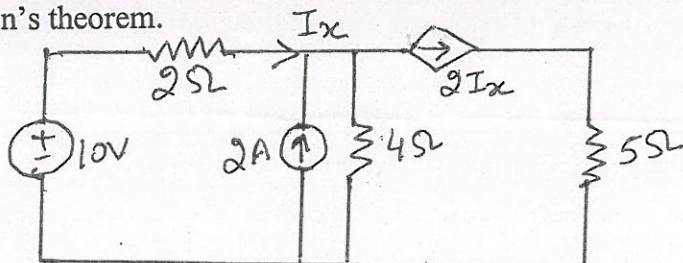- Q2. State and prove reciprocity theorem.
- Q3. What is an ideal transformer? Draw its phasor diagram.
- Q4. What is a transfer function & what is its importance? What are poles and zeros of a transfer function?
- Q5. An impedance of $(3+j5)\Omega$ is connected across a 10V, 50Hz source. Find i) Power factor (ii) Real and reactive power (iii) Current drawn by impedance.
- Q6. Find the current through the 2Ω resistor using Norton's theorem. Verify the result by Thevenin's theorem.



P.T.O

Q7. Distinguish between Series and parallel resonance for AC circuits.

[Marks: 12 each]

Part C

Q8. State and prove maximum power transfer theorem for AC circuits.

OR

What is a) Superposition Theorem b) Compensation Theorem c) Mesh Analysis.

Q9. Realise the function

$$Z(s) = \frac{s(s^2+10)}{(s^2+4)(s^2+16)}$$

in both the Foster first and second forms.

OR

Find the current ratio (I_1/I_2) in the given circuit. Also find Y parameters.

